



1. **Identify the components** of the system shown in the diagram.
 2. **Describe the function** of each component.
 3. **Explain the overall operation** of the system.
 4. **Discuss the advantages** of this design.
 5. **Propose improvements** to the system.

QUESTION