

QUESTION 4 (10%)

Calculate the average number of times the following circuit will be executed.

